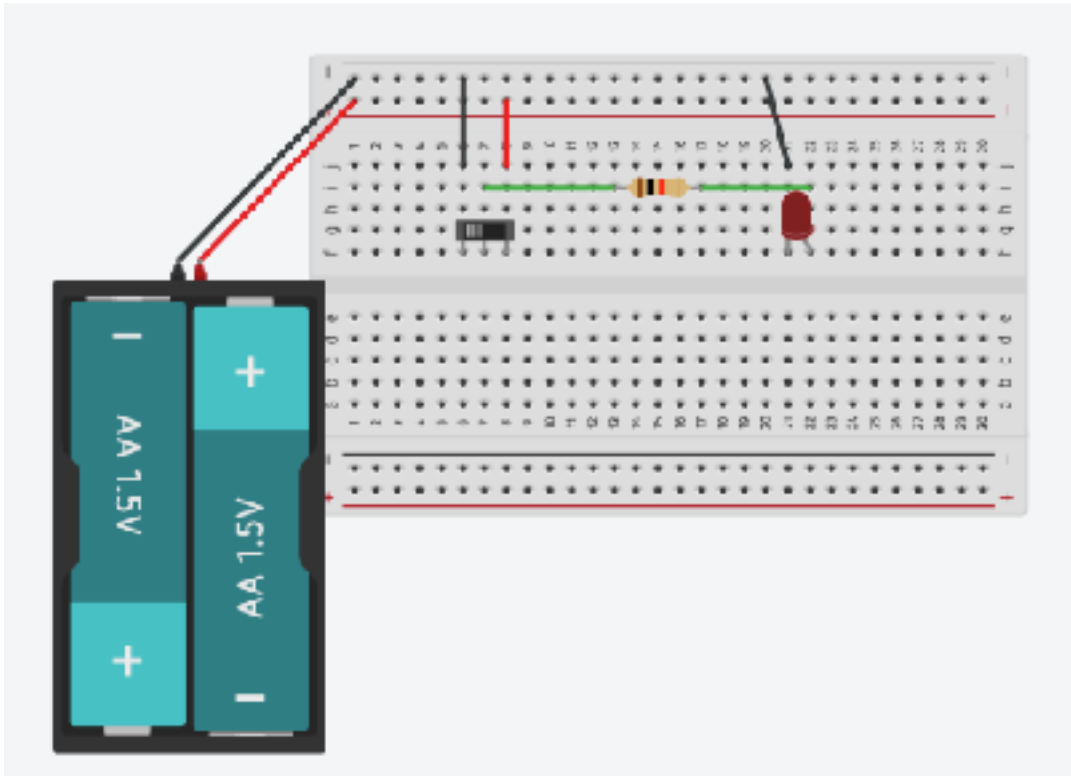


19AIE103 – Introduction to Drones

Lab Worksheet – 1

Introduction to Tinkercad - Electronics Module


1. Design a circuit to control a LED with on/off switch



Points to learn

- Connecting different components using wires
- Using a breadboard
- Customizing the circuit like, naming the components, changing wire colors etc.
- Working of an on/off switch

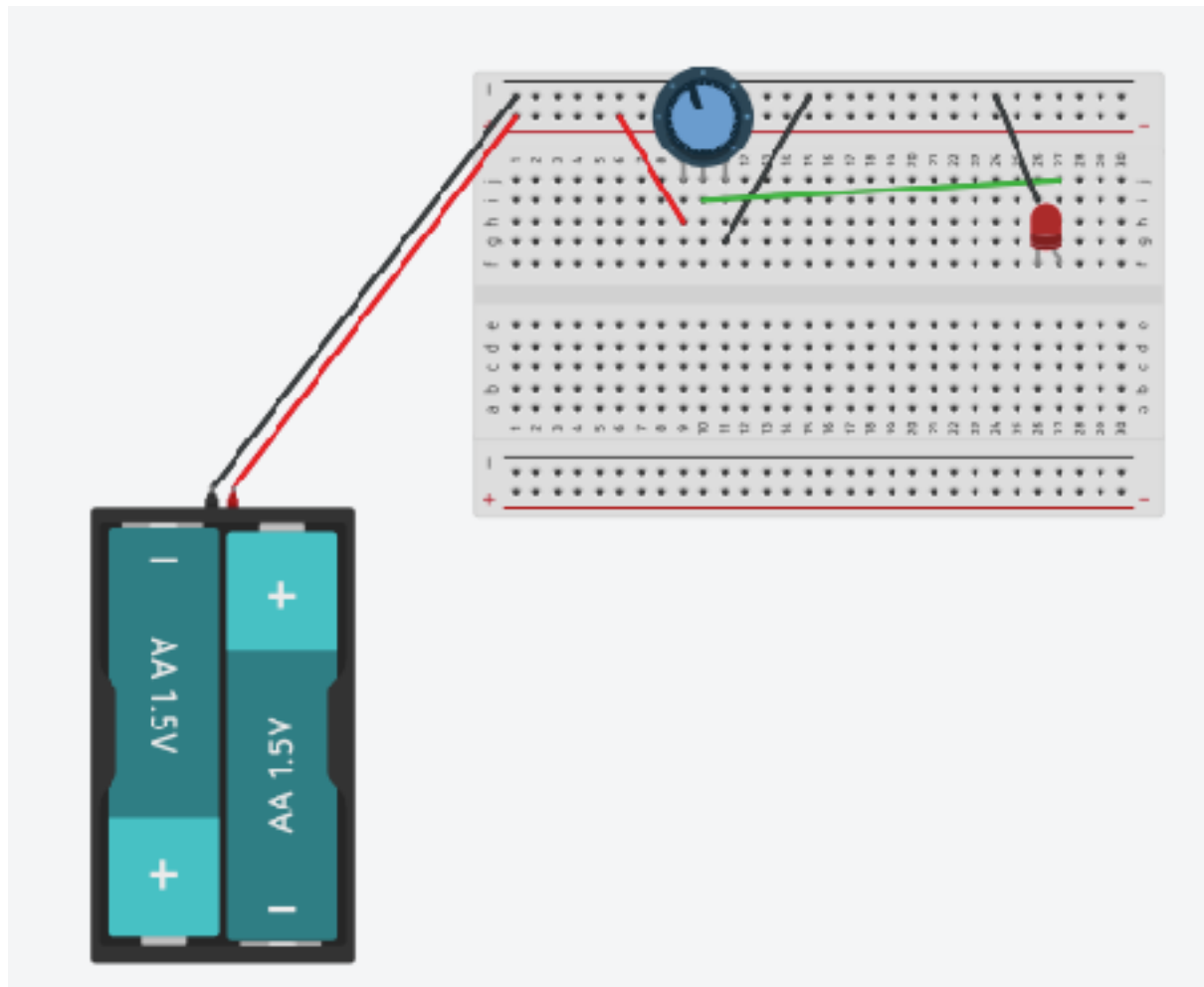2. Design a circuit to control the brightness of LED using potentiometer



Points to learn

- Working principal of potentiometer
- Role of current in light brightness control

Assignment

1. Design a circuit to implement two way switch connection to control an LED. The solution file should adhere to the following instructions.
 - a. Use the given format
 - b. Paste a clearly visible snap of your circuit with your register number in the format "BL.EN.U4AIE20XXX"
 - c. Snapshot of all the possible output cases with your file name clearly visible.