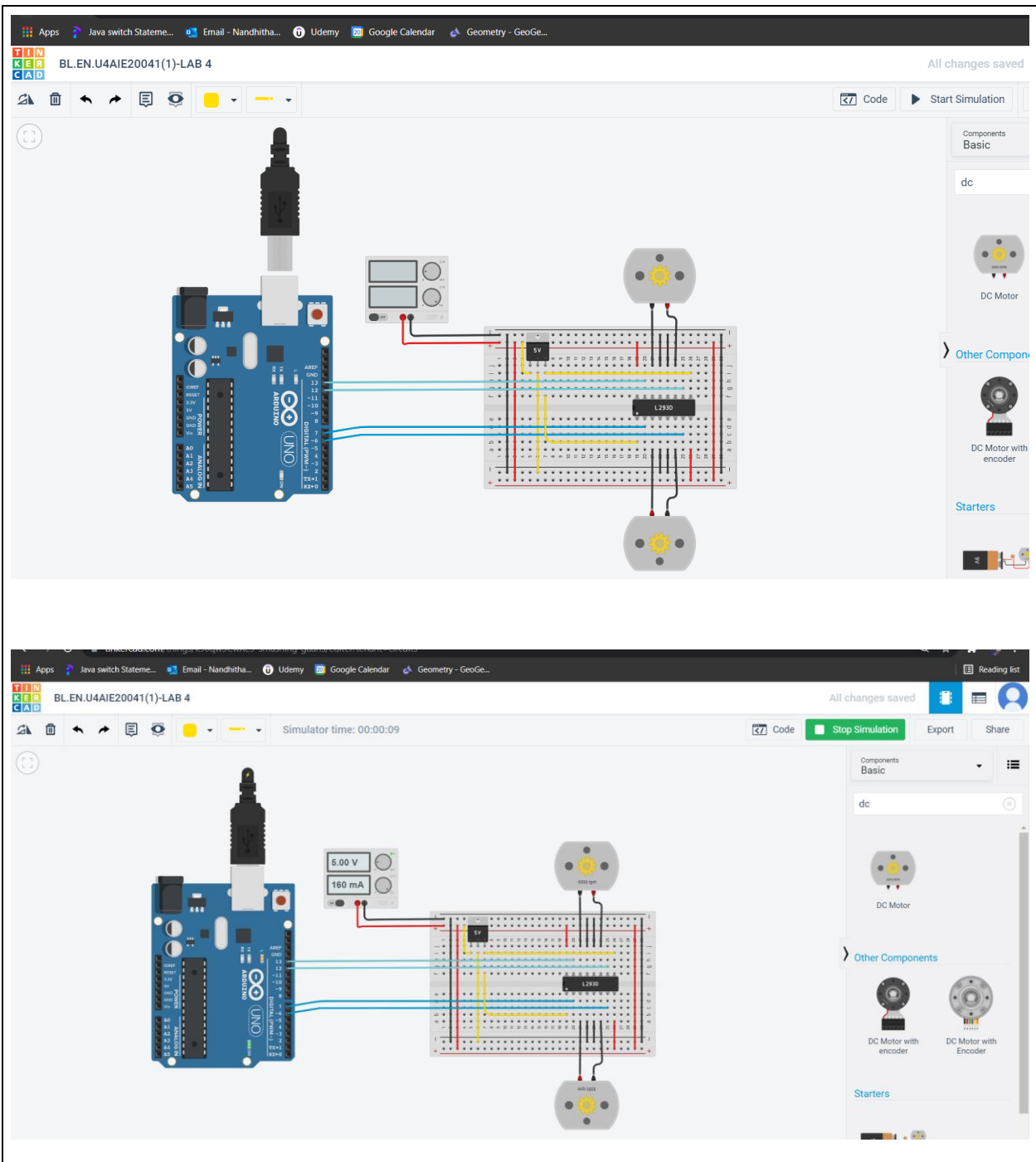


## 19AIE102 – Introduction to Drones

### Lab Submission



1. Design a circuit and write an program to interface and actuate two DC motors using L293D and Arduino.



Reg No:


Name:

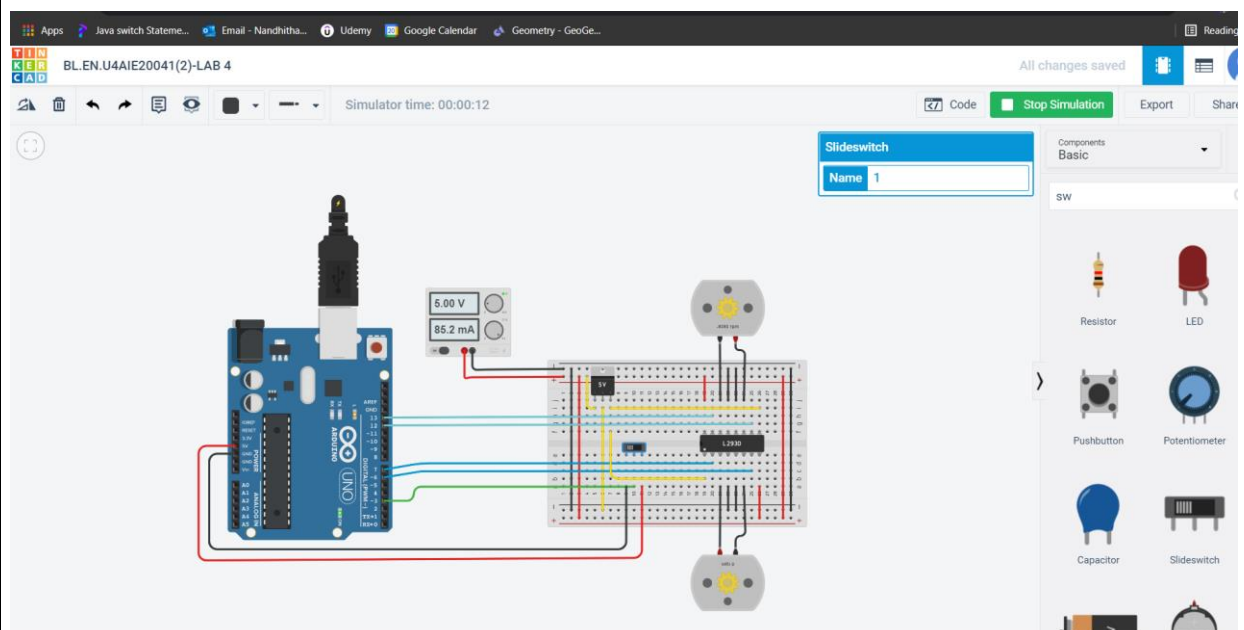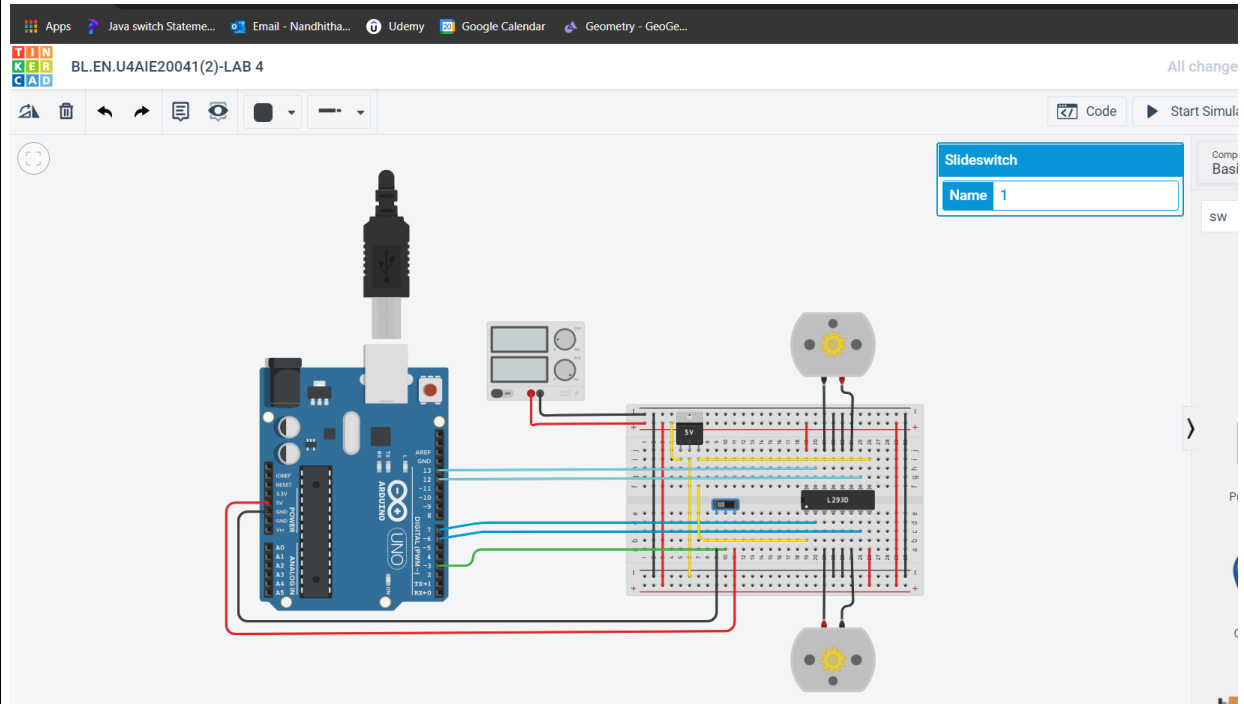2) Interface a switch and write an Arduino program for the above circuit to control the motor actuation using a switch. If the switch is on motor in channel 1 should run else motor in channel 2 should run



Reg No:

Name:

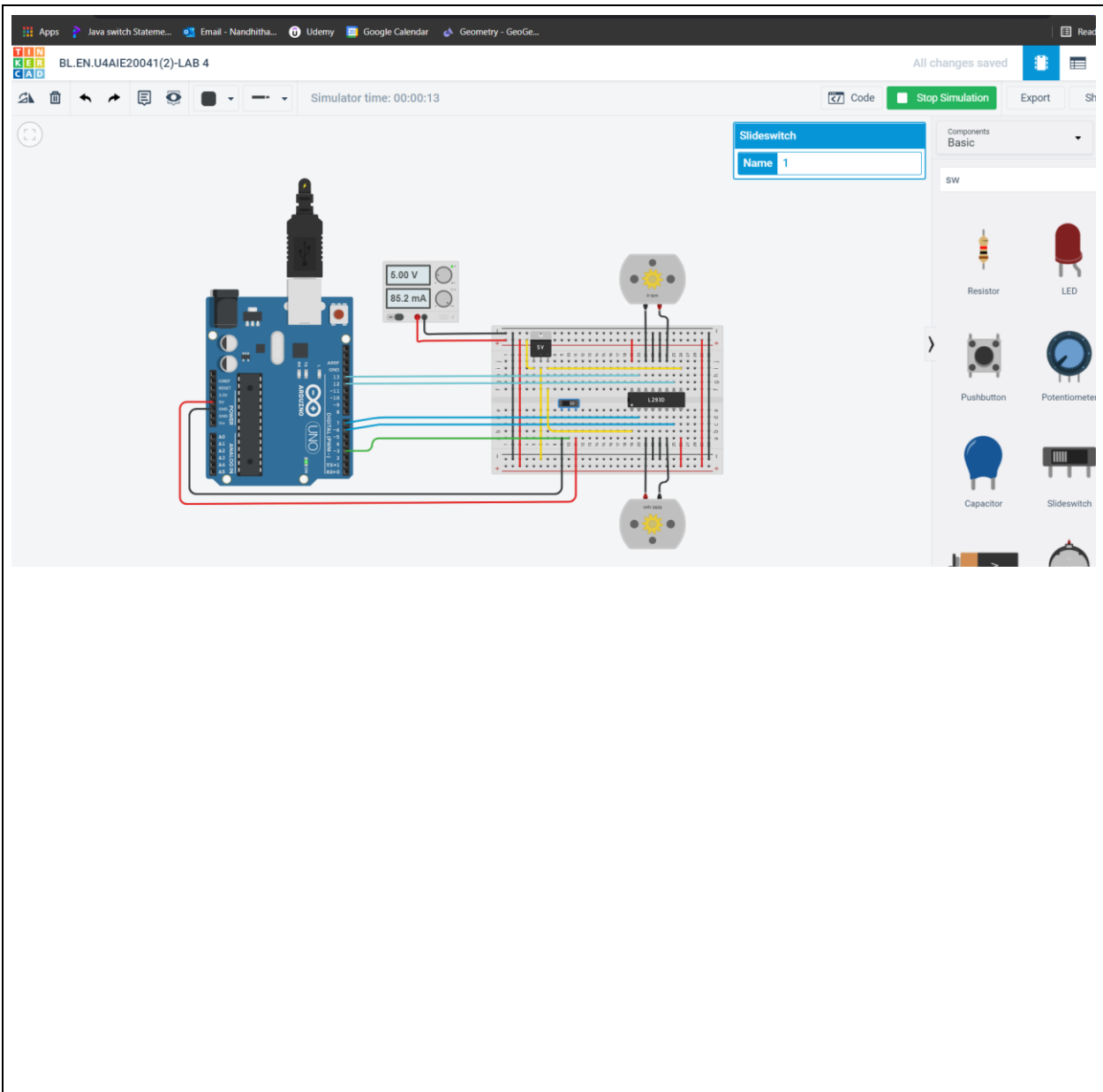

a.

Reg No:

Name:

Output snapshot with file name clearly visible